

SARKAR, Mohul

Experiment Number 7

Op Amp Circuits

TUESDAY

April 9

ECE 1101L

Spring 2024

Partner Name(s): MARIN, Gregorio

Lab:

ECE 1101L Experiment 7

OP AMP CIRCUITS

OBJECTIVES


MATERIALS REQUIRED BY STUDENT

- 11 clip leads
- A breadboard plus jumper wires
- Required Resistors

MATERIALS TO BE SUPPLIED

- Multimeter S/N: MY50210029
- Oscilloscope S/N: MY50512828
- Waveform Generator S/N: MY48008120
- Power Supply S/N: MY51110030

Pre-lab:

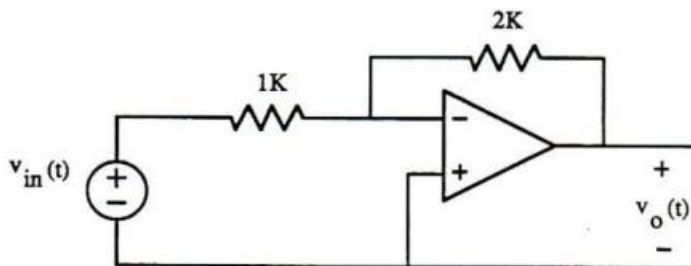


Calculate – assuming the op amp is ideal

- The gain $G = v_o/v_{in}$
- The input resistance R_{in} as seen from the source

To calculate gain I use the equation and plug in my values and since it's an inverting op amp. From this I get, $V_o / V_{in} = -2k\Omega / 1k\Omega = -2 = A_v$.

$$R_{in} = V_{in} / I_{in} = 1k$$

B)

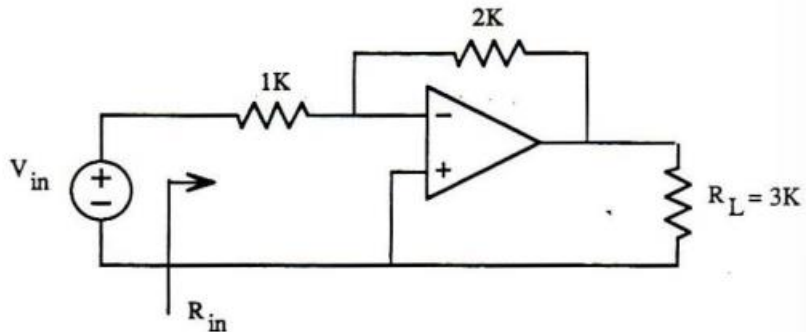


$$V_x = V_T / 3$$

$$I_T = V_T / 3 \text{ k}\Omega + (V_T - 10^5 V_x) / 75 + V_T (1 + 10^5 (1/3)) / 75$$

$$I_T = V_T / 3 \text{ k}\Omega + V_T [1 + (10^5/3)] / 75$$
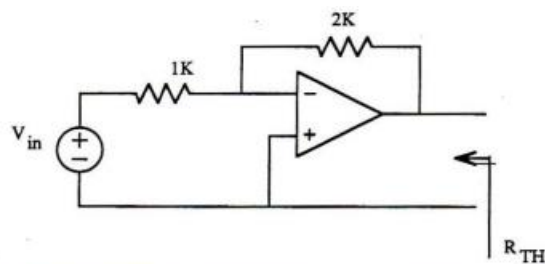
$$V_T / I_T = 1 / (1/3k) + (10^5/3) / 75 = 2.25 \text{ m}\Omega$$



Do not calculate R_{TH} by actually shorting V_{in} and putting a source at the output. See Section 3.3.5 of Chapter 3 to see how to calculate R_{TH} with V_{in} present and a known load R_L connected at the output. Assume $R_o = 75 \Omega$ and $A = 10^5$

2. Design a positive gain op amp circuit with gain

$$G = \frac{V_o}{V_{in}} = (\text{Birthday})^{1/4}$$

where by Birthday is meant the date of your birth (from 1 to 31). Assuming the op amp in your circuit is ideal calculate the

- Input resistance R_{in} of your circuit as seen by the source
- Thevenin Equivalent output resistance R_o of your circuit as seen by the load

2a)


My birthday is August 16th

$$G = (V_o/V_{in}) = (16)^{1/4} = 2$$

$$R_f = 10 \text{ k}\Omega$$

Current entering the op-amp is 0, so resistance seen by source is infinite.

3. Given the three circuits

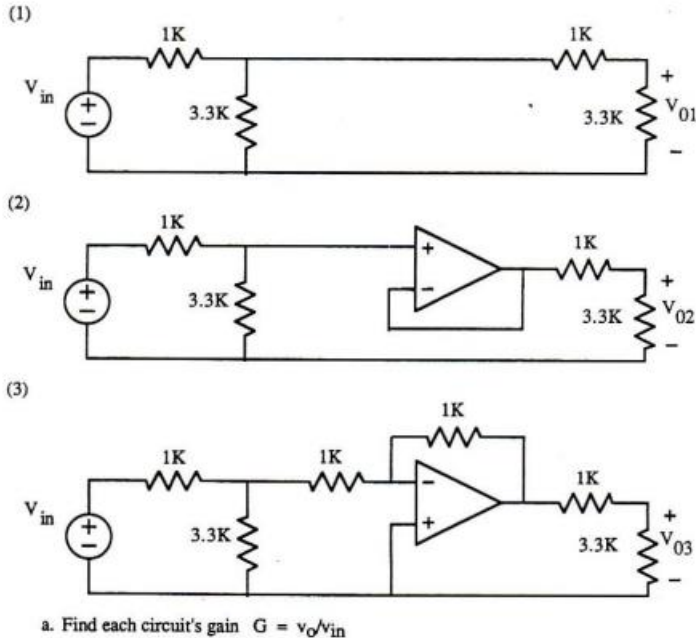

3a)

Node V: Use nodal analysis to get both values then divide to get gain

$$V - V_{in}/1 \text{ k}\Omega + V/3.3\text{k} + V/(1 \text{ k}\Omega + 3.3 \text{ k}\Omega) = 0$$

$$V(1.5365) = V_{in}$$

$$V = 0.651V_{in}$$

$$V_{01} = V * 3.3 \text{ k}\Omega / 3.3 \text{ k}\Omega + 1 \text{ k}\Omega = 0.499$$

3b)

Node V: Use voltage divider to simplify circuit then use again to find both voltages then divide to get gain

$$V_p = (3.3 \text{ k}\Omega / 1 \text{ k}\Omega + 3.3 \text{ k}\Omega)V_{in}$$

$$V_p = 0.767V_{in}$$

$$V_0 = V_p$$

$$V_{02} = (3.3 \text{ k}\Omega / 1 \text{ k}\Omega + 3.3 \text{ k}\Omega)0.767V_{\text{in}}$$

$$V_{02}/V_{\text{in}} = 0.589$$

3c)

Node V1: use nodal analysis to get voltages then use voltage divider to solve for V_{03} . Then divide that value by V_{in} to get gain.

$$V_1 - V_{\text{in}} / 1 \text{ k}\Omega + V_1 / 1 \text{ k}\Omega + V_1 / \text{k}\Omega = 0$$

$$V_1(1 + 1/3.3 + 1) - V_{\text{in}} = 0$$

$$V_1 = 0.434V_{\text{in}}$$

$$V_p = V_n = 0$$

$$V_p - V_1 / 1 \text{ k}\Omega + -V_0 / 1 \text{ k}\Omega = 0$$

$$V_0 = -V_1$$


$$V_0 = -0.434 \text{ V}$$

$$V_{03} = (3.3 \text{ k}\Omega / 1 \text{ k}\Omega + 3.3 \text{ k}\Omega)V_0$$

$$V_{03} = 3.3 \text{ k}\Omega / 4.3 \text{ k}\Omega * (-0.434V_{\text{in}})$$


$$V_{03}/V_{\text{in}} = -0.333$$

Given CKT2:

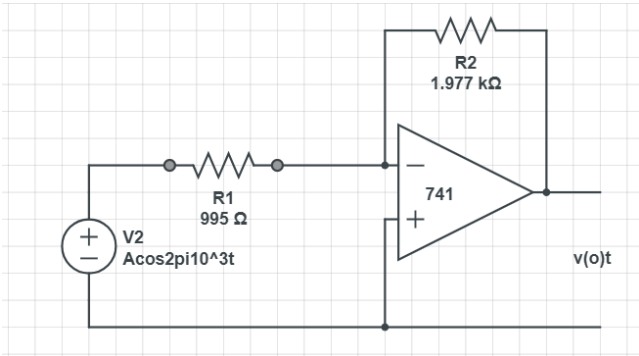


A)


Per sign convention shown on CKT1		
Voltages [V]	A V_{in} [V]	A V_{out} [V]
5	10.1	19.5
6	11.9	22.9
7	13.7	26.5
8	15.7	28.3
9	17.5	28.3

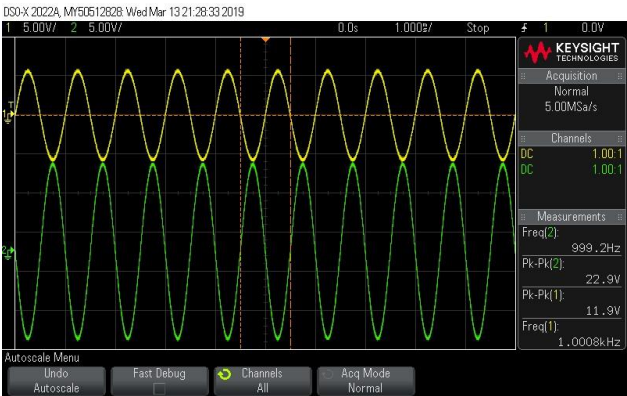

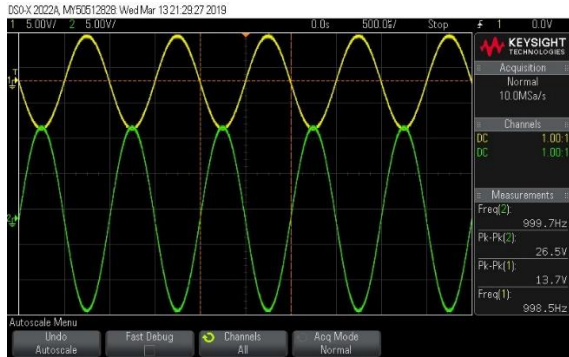
$Pk-pk(1) = 11.9 \, V$, $Pk-pk(2) = 22.9 \, V$



Pk-Pk(1) = 13.7 V, Pk-Pk(2) = 26.5 V

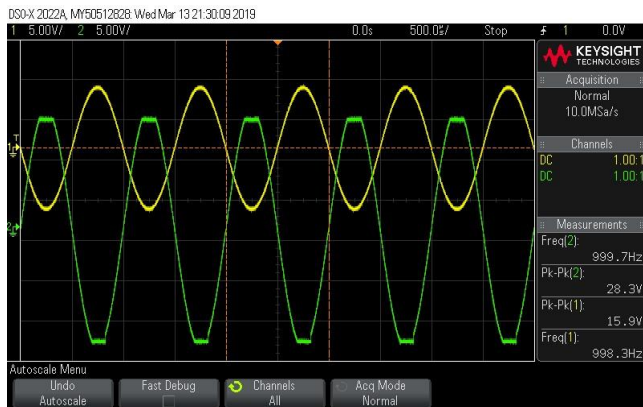

Pk-Pk(1) = 15.9 V, Pk-Pk(2) = 28.3 V

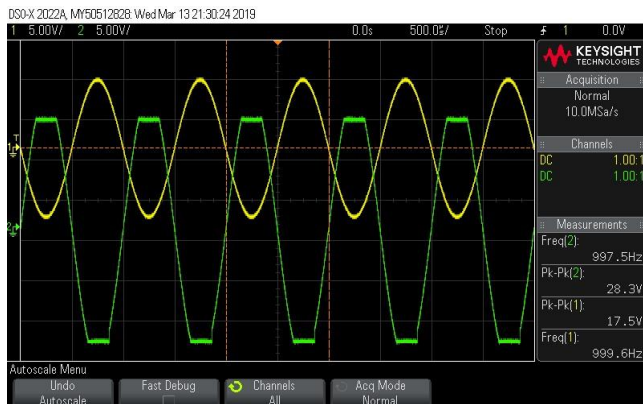

Pk-Pk(1) = 17.5 V, Pk-Pk(2) = 28.3 V

B)

$$1 \text{ V} / 1 \text{ mA} = 1 \text{ k}\Omega$$

The input resistance as seen by the source while $A_{vin} = 1 \text{ V}$ is $R_{in} = 1 \text{ k}\Omega$

C)

Short circuit

Add 2.2k resisor (2.17k Ω real value)

$$V_o = V_{th} = 19.1 \text{ V}$$

$$V_L = V_{RL} = 19.3 \text{ V}$$


$$R_{th} = (V_{th} - V_{2.17k\Omega}) / I_{2.17k\Omega}$$

D)

With $A_{v(in)} = 5$ V these are the measurements to verify the op amp input is a virtual short:

$$V_p = 74 \text{ mV}, V_n = 78 \text{ mV} = \sim 0$$

Given CKT4:

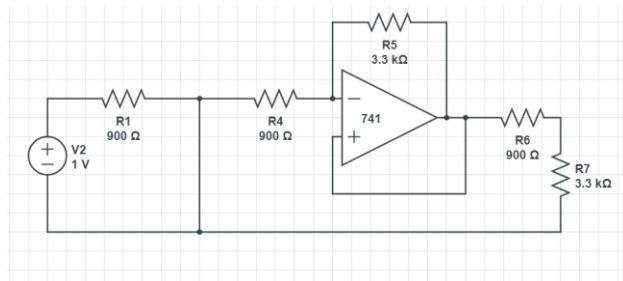

Measured resistor values: $R_{3.3k} = 3.3k$, $R_{3.3k} = 3.3k$, $R_{0.9k} = 0.9k$, $R_{0.9k} = 0.9k$

Gain for number 3a) 518 mV

Gain for number 3b) 560 mV

Gain for number 3c) 400 mV

Discussion of Results:

My results from the lab have shown that I have properly learned to find the gain of an op-amp. I have also learned how the specific pins of an op-amp work to make mathematical calculations and to amplify the voltage it receives. Another thing I learned was that not only do you need to put power into the part which converts the value, but you must also put power into the op-amp itself. I am confident now in being able to utilize op-amps in my future circuits and understand how they can create a virtual short.

Post Lab:

3.19)

We know in finding Thevenin equivalent we need to find Thevenin voltage and Thevenin resistance.

Thevenin Voltage:

Using KCL:

$$(V_{th} - V_{in}) / 1k\Omega + V_{th} / 1k\Omega + V_{th} / 1k\Omega + 10I_1 = 0$$

$$I_1 = V_{th} / 1k\Omega = V_{th}$$

$$(V_{th} - V_{in}) / 1k\Omega + V_{th} / 1k\Omega + V_{th} / 1k\Omega + 10V_{th} = 0$$

$$V_{th} = V_{in} / 13$$

To find the Thevenin equivalent resistance you must remove the dependent source then apply a test voltage and current.

Using KCL:

$$V / 1k\Omega + V / 1k\Omega + V - V_x / 1k\Omega = 0$$


$$V = V_x / 3$$

$$V_x - V / 1k\Omega + 10I_1 + V_x / 1k\Omega = I_x$$

$$2V_x + 3V_x = I_x$$

$$V_x = I_x / 5$$

$$R_{th} = 1/5 = 0.2k\Omega$$

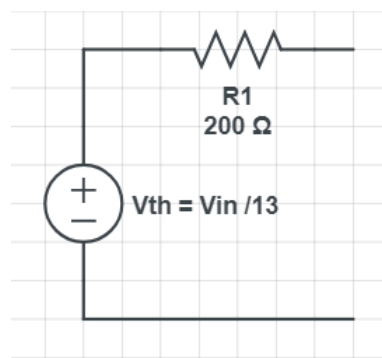

3.20)

Thevenin Voltage:

Using KCL:

$$(V - \text{cost}) / 1\text{k}\Omega + V / 1\text{k}\Omega + (V - V_{\text{th}}) / 1\text{k}\Omega + 2I_2 = 0$$

$$I_1 = \text{cost} - V$$

$$2V = V_{\text{th}} - I_1$$

$$2V = V_{\text{th}} - \text{cost} + V$$

$$V = V_{\text{th}} - \text{cost}$$

$$V_{\text{th}} = V + 2I_1$$

$$V_{\text{th}} = V + 2(\text{cost} - V)$$

$$V_{\text{th}} = (3/2)\text{cost}$$

Thevenin Resistance:

Using KCL:

$$V / 1\text{k}\Omega + V / 1\text{k}\Omega + V - V_x / 1\text{k}\Omega + 2I_1 = 0$$

$$I_1 = -V$$


$$3V = V_x - 2(-V)$$

$$I_x = (V_x - V) / 1\text{k}\Omega - 2I_2$$


$$I_x = V_x - V - 2I_2$$

$$I_x = 2V_x$$
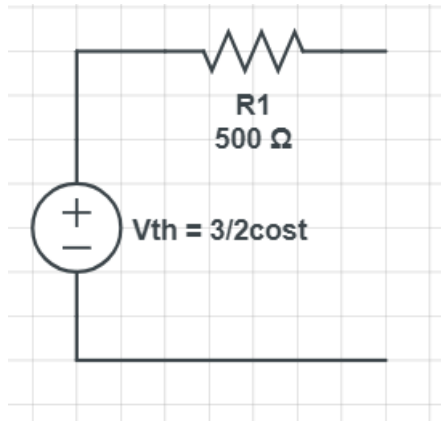
$$R_{\text{th}} = V_x / I_x = 1/2 = 0.5\text{k}\Omega$$



3.31)

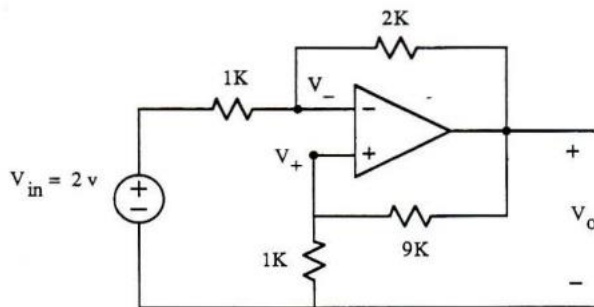

a) No input terminal is directly grounded so $+V = -V$. feedback is also taken to non-inverting terminal.

b) $(V_2 - 2) / 1 \text{ k}\Omega + (V - V_o) / 2 \text{ k}\Omega = 0$

$$V[1.5 * 10^{-3}] - 2 * 10^{-3} = V_o / \text{k}\Omega$$


$$V_o / 9\text{k}\Omega + V / 1\text{k}\Omega = 0$$

$$V_o / 9\text{k}\Omega = V[1/9000 + 1/1000]$$

$$10 \text{ V} = 3 \text{ V} - 4$$

$$V = -0.5714 \text{ V}$$

c) Remove $9\text{k}\Omega$ resistor

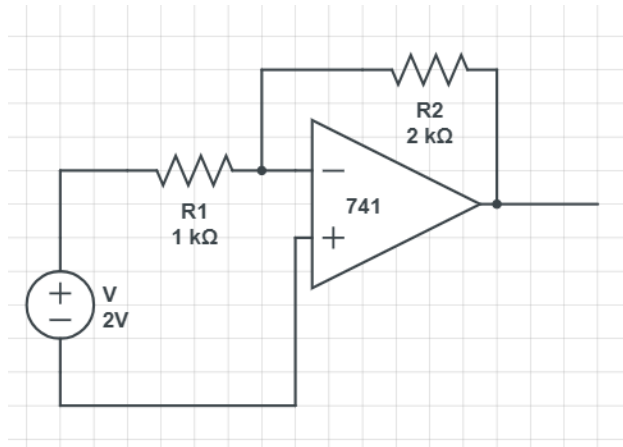

3)

$$R_{in1} = R_{in2} = R_{in3} = R_{out}$$

$$V_{in1} = V_n * R_{in} / R_{in} + R_{in} = A_{v(in)} [R_{in} / R_{in} + R_{out}] V_{in}$$

$$V_{in3} = A_{v(in)2} * R_{in} / R_{in} + R_{out} = A^3/2 [(R_{in} * R_2) / (R_{in} + R_{out})^2 (R_2 + R_{out})] V_{in}$$

$$V_{out} / V_{in} = A^3/2 [R_{in} / R_{in} + R_{out}]^2 R_{in} / R_{in} + R_{out}$$

4)

Node 1:

$$V_{in} / 1k\Omega$$

$$V = -10V_{in}$$

Node 2:

$$-[V/10 k\Omega + V/100 + V / 10 k\Omega] = -V_0 / 10 k\Omega$$

$$V_0 = 102 V_{in}$$

$$V_0 / -10V_{in} = -102$$

$$V_0 / V_{in} = -1020 = \text{Gain}$$